

# A Brief about Ripple Counter with Circuit Timing Diagrams

While carefully observing the production line of glass bottles, which were being packed package by machines, an inquisitive mind questions – How does the machine knows to of bottles? What teaches the machines how to count? Searching an answer to solve this to a very interesting invention named – “**Counter’s**”. Counters are the circuit which c clock pulses. These are usually designed using flip-flops. Based on the way clock i functioning counters are classified as **Synchronous and Asynchronous counters**. In look at an Asynchronous counter which is notoriously known as **Ripple counter**.

## What is a Ripple Counter?

Before jumping to Ripple Counter let's get familiarized with the terms **Synchronous and counters**. Counters are circuits made using flip-flops. Synchronous counter, as the name suggests, has all **the flip-flops** working in sync with clock pulse as well as each other. Here clock pulse is applied to every flip flop.

Whereas in Asynchronous counter clock pulse is applied only to the initial flip flop which is considered as LSB. Instead of the clock pulse, the output of first flip-flop acts as a clock for the next flip flop, whose output is used as a clock to the next in line flip-flop and so on.

Thus, in Asynchronous counter after the transition of the previous flip flop transition occurs, the next transition takes place, not at the same time as seen in Synchronous counter. Here flip-flops are in a Master-Slave arrangement.

**Ripple Counter:** Ripple counter is an Asynchronous counter. It got its name because the clock signal ripples through the circuit. An n-MOD ripple counter contains n number of flip-flops and can count up to  $2^n$  values before it resets itself to the initial value.

These counters can count in different ways based on their circuitry.

**UP COUNTER:** Counts the values in ascending order.

**DOWN COUNTER:** Counts the values in descending order.

**UP-DOWN COUNTER:** A counter which can count values either in the forward or reverse direction is called an up-down counter or reversible counter.

**DIVIDE by N COUNTER:** Instead of a binary, we may sometimes require to count up to 10. A ripple counter which can count up to value N which is not a power of 2 is called a Divide-by-N counter.




## Ripple Counter Circuit Diagram and Timing Diagram

The **working of the ripple counter** can be best understood with the help of an example. A number of flip-flops used there are 2-bit, 3-bit, 4-bit..... ripple counters can be designed. We will look at the working of a 2-bit **binary ripple counter** to understand the concept.

A **binary counter** can count up to 2-bit values .i.e. **2-MOD counter** can count  $2^2 = 4$  values. If the value is 2 we use 2 flip-flops. While choosing the type of flip-flop it should be remembered that ripple counters can be designed only using those flip-flops which have a condition for toggling. We will use **JK flip-flops**.
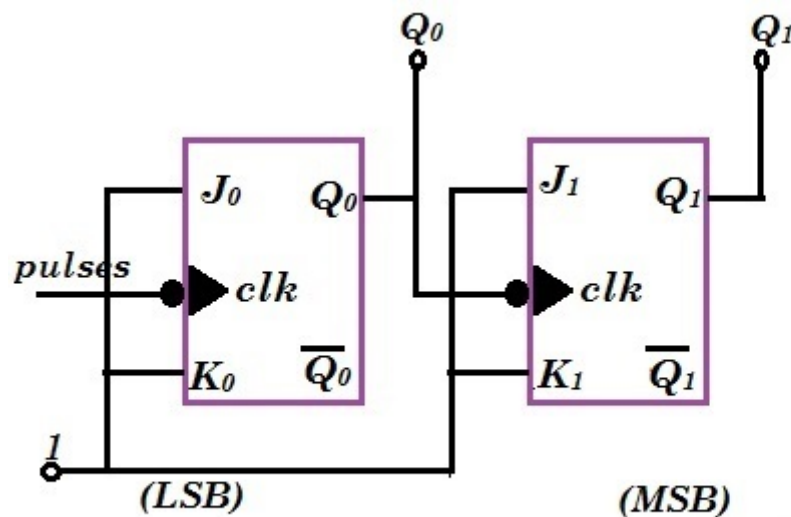
### Binary Ripple Counter using JK Flip Flop

The circuit arrangement of a **binary ripple counter** is as shown in the figure below. Here two JK flip-flops are used. JK inputs of flip-flops are supplied with high voltage signal maintaining them in state 1. The symbol for the clock pulse indicates a negative triggered clock pulse. From the circuit, it can be observed that the output Q0 of the first flip-flop is applied as a clock pulse to the second flip-flop.



©Elprocus.com


Binary Ripple Counter Using JK Flip Flop

Here the output  $Q_0$  is the LSB and the output  $Q_1$  is the MSB bit. The functioning of the counter can be easily understood using the Truth Table of JK flip flop.

$J_n$	$K_n$	$Q_{n+1}$
0	0	$Q_n$
1	0	1
0	1	0

1	1	$Q_n$
---	---	-------

So, according to the Truth table, when both the inputs are 1 the next state will be the previous state. This condition is used in ripple flip flop. As we have applied a high value to the inputs of flip-flops they are at the state 1, so they must toggle the state at the negative clock pulse .i.e. at the transition 1 to 0 of the clock pulse. The timing diagram of the binary ripple counter clearly explains the operation.

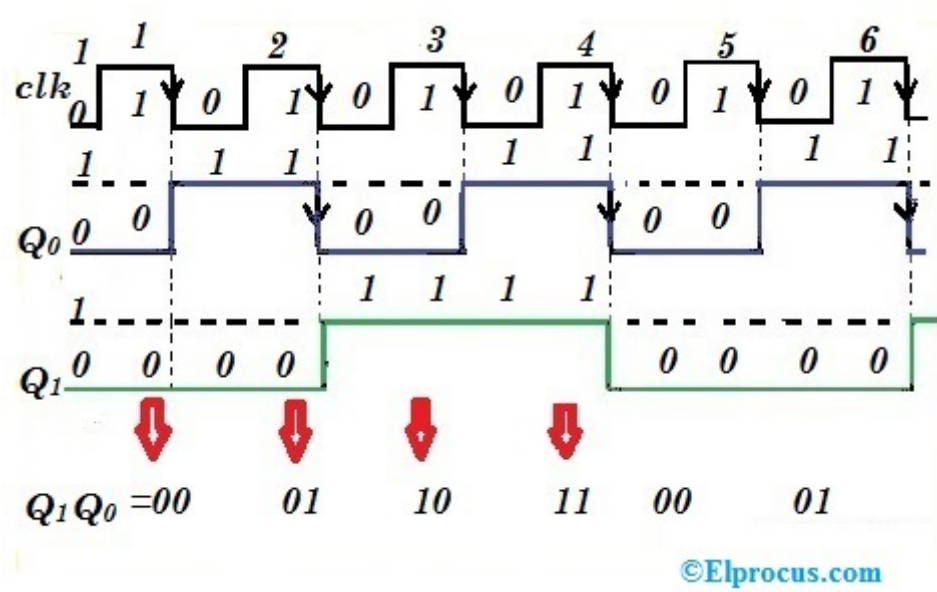

Timing Diagram of Binary Ripple Counter


From the timing diagram, we can observe that Q0 changes state only during the negative-going transition of the applied clock. Initially, the flip flop is at state 0. Flip-flop stays in the state until the applied clock transitions from 1 to 0. As the JK values are 1, the flip flop should toggle. So, it changes state from 0 to 1 and continues for all pulses of the clock.

Number of input pulses	Q <sub>1</sub>
0	—
1	0
2	0
3	1

Coming to the second flip flop, here the waveform generated by flip flop 1 is given as c we can see in the timing diagram when Q0 goes transition from 1 to 0 the state of Q1 changes. Consider the above clock pulse, only follow the waveform of Q0. Note that the output Q0 is considered as LSB and Q1 are considered as MSB. From the timing diagram, we can see the counter counts the values 00,01,10,11 then resets itself and starts again from 00,01,... are applied to JK flip flop.

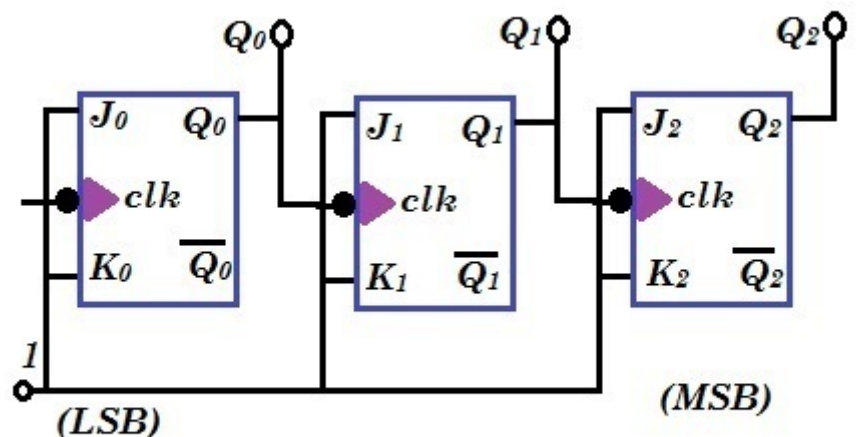
### 3-bit Ripple counter using JK flip-flop – Truth Table/Timing Diagram

In the 3-bit ripple counter, three flip-flops are used in the circuit. As here 'n' value is three, it counts up to  $2^3 = 8$  values .i.e. 000,001,010,011,100,101,110,111. The circuit diagram are given below.



©Elprocus.com

Binary Ripple Counter Using JK Flip Flop

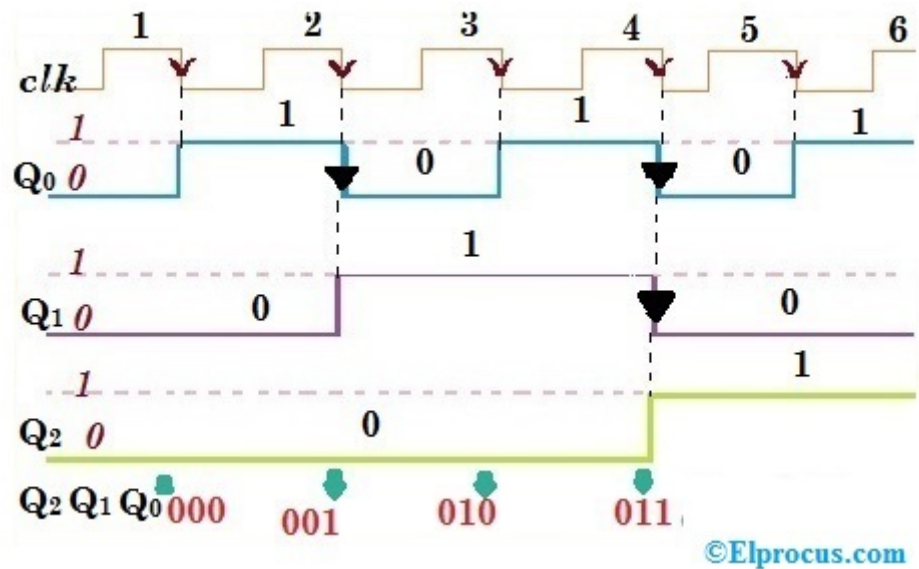


3 bit Ripple Counter Timing Diagram

Here the output waveform of Q<sub>1</sub> is given as clock pulse to the flip flop J2K2. So, when Q<sub>1</sub> transitions, the state of Q<sub>2</sub> is changed. The output of Q<sub>2</sub> is the MSB.

Number of pulses	Q <sub>2</sub>	Q <sub>1</sub>
0	—	—
1	0	0
2	0	0
3	0	1
4	0	1
5	1	0
6	1	0
7	1	1
8	1	1

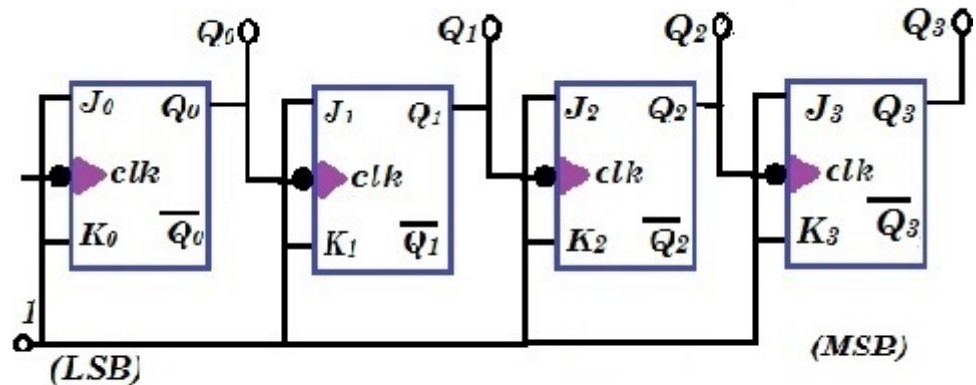
## 4-bit Ripple Counter Using JK Flip flop – Circuit Diagram and Timin

In 4-bit ripple counter, n value is 4 so, 4 JK flip flops are used and the counter can count from 0 to 15. Below the **circuit diagram** and **timing diagram** are given along with the truth table.



©Elprocus.com

4 bit Ripple Counter using JK Flip Flop

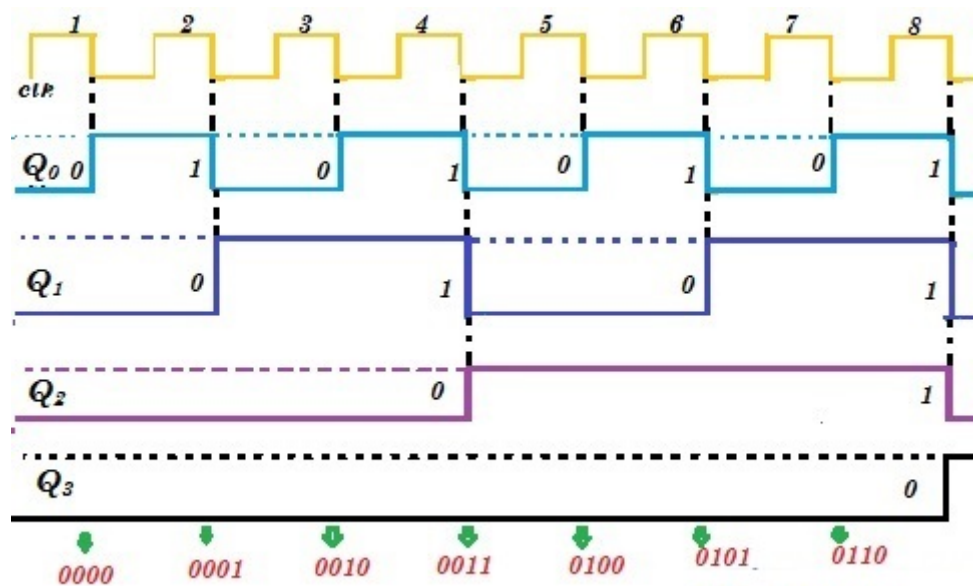

©Elprocus.com

4 bit Ripple Counter Timing Diagram

## 4 bit Ripple Counter Using D Flip Flop

When it comes to selecting a Flip Flop for Ripple counter designing an important point to note is that the flip flop should contain a condition for toggling of states. This condition is satisfied by JK flip flops.


From the truth table of **D flip flop**, it can be clearly seen that it doesn't contain the toggle condition. When a D flip flop is used as a Ripple counter, it has an initial value of 1. When the clock pulse is applied, the output Q becomes 0. This process repeats itself for every clock pulse.



transition from 1 to 0 the flip flop should change the state. But according to truth table it stays on 1 until D value is changed to 0. So, the waveform of D0-flip flop will always stay at 1 for counting. So, D flip flop is not considered for construction of Ripple Counters.
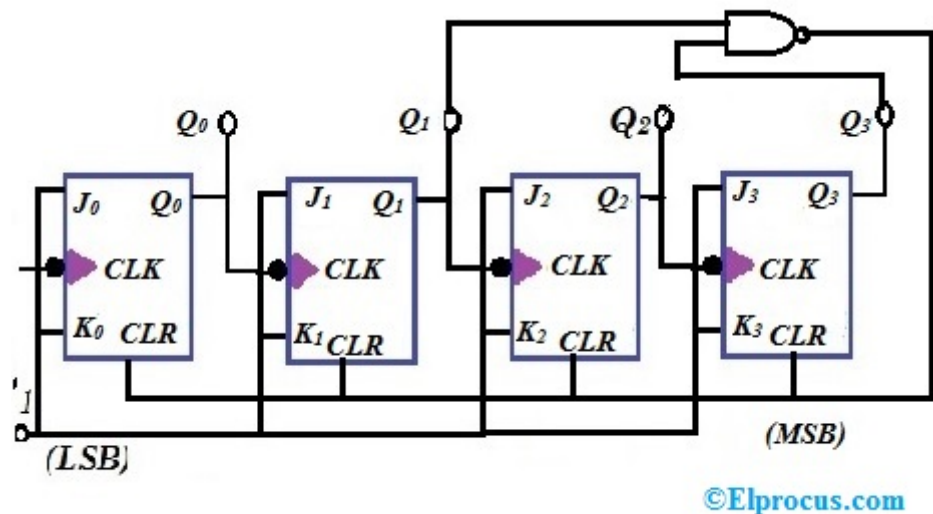
## Divide by N counter

Ripple counter counts values up to  $2^n$ . So, to count values which are not powers of 2 is **the circuitry** that we have seen till now. But by modification, we can make ripple counter which cannot be expressed as a power of 2. Such a counter is called **Divide by N counter**.



Decade Counter

The number of flip flops  $n$  to be used in this design are chosen in such a way that  $2^n >$  count of the counter. Along with flip flops, a feedback gate is added so that at count  $N$  it resets to zero. This feedback circuit is simply a **NAND gate** whose inputs are the outputs of the flip flops whose output  $Q = 1$  at the count  $N$ .

Let us see the circuit of a counter for which  $N$  value is 10. This counter is also known as a decade counter as it counts up to 10. Here the number of flip flops should be 4 because of  $2^4 = 16 > 10$ . For  $N = 10$  the outputs  $Q_1$  and  $Q_3$  will be 1. So, these are given as inputs to the NAND gate. The output of the NAND gate is applied to all the flip flops thereby resetting them to zero.

## Drawbacks of Ripple Counter

The carry propagation time is the time taken by a counter to complete its response to a clock pulse. As in ripple counter, the clock pulse is Asynchronous, it requires more time

response.

## Applications of Ripple Counter

These counters are frequently used for measurement of Time, Measurement of Frequency of Distance, Measurement of Speed, Waveform generation, Frequency Division, Digital Counting etc....

Thus this is all about **brief information about ripple counter**, the working of binary counters construction using JK-Flip Flop along with circuit diagram, **ripple counter** and truth table. The main reason behind the construction of the ripple counter disadvantages and applications of Ripple Counter. here is a question for you, what is a **Counter?**

### SHARE THIS POST:

[Facebook](#)[Twitter](#)[Google+](#)[LinkedIn](#)[Pinterest](#)[◀ PREVIOUS](#)

IC DAC0808: Pin Configuration, Circuit Diagram and Applications

Introduction to Application Specific

### RELATED CONTENT



2SA1015 Transistor : Pin Configuration & Its Applications



CMOS OV7670 Camera Module : Working & Its Applications



DS1990A iButton : Pin Configuration & Its Applications



1N914 Diode : Pin Configuration & Its Applications

**Add Comment**

Comment:

Name \*

Email \*

Website

Post Comment

## CATEGORIES

Communication

Electrical

Electronics

Project Ideas

Robotics

Technology

## RECENT COMMENTS

Tarun Agarwal on Introduction to Fiber Optic Sensors and their Types with Applications

Tarun Agarwal on IEEE Projects on Embedded Systems

Anki on IEEE Projects on Embedded Systems

Sudipta Panigrahy on Introduction to Fiber Optic Sensors and their Types with Applications

Copyright 2013 - 2021 © Elprocus

