

DiS Notes (divB):- ODD 2020-2021

(Author: Prof Ravindra Divekar)

Here is the list of rules used for the boolean expression simplifications. This is a fairly standard list you could find most anywhere, but we thought you needed an extra copy.

The Idempotent Laws	$AA = A$	$A+A = A$
The Associative Laws	$(AB)C = A(BC)$	$(A+B)+C = A+(B+C)$
The Commutative Laws	$AB = BA$	$A+B = B+A$
The Distributive Laws	$A(B+C) = AB+AC$	$A+BC = (A+B)(A+C)$
The Identity Laws	$AF = F$ $AT = A$	$A+F = A$ $A+T = T$
The Complement Laws	$A\bar{A} = F$ $A+\bar{A} = T$	$\bar{\bar{F}} = T$ $\bar{\bar{T}} = F$
The Involution Law	$\bar{\bar{A}} = A$	
DeMorgan's Law	$\overline{AB} = \bar{A} + \bar{B}$	$\overline{A+B} = \bar{A} \bar{B}$

Simplify: $C + BC$:

<u>Expression</u>	<u>Rule(s) Used</u>
$C + BC$	Original Expression
$C + (B + C)$	DeMorgan's Law.
$(C + C) + B$	Commutative, Associative Laws.
$T + B$	Complement Law. (T means true or logic1)
T	Identity Law.(T=1)

Simplify: $AB(A + B)(B + B)$:

<u>Expression</u>	<u>Rule(s) Used</u>
$AB(A + B)(B + B)$	Original Expression
$AB(A + B)$	Complement law, Identity law.
$(A + B)(A + B)$	DeMorgan's Law
$A + BB$	Distributive law. This step uses the fact that "or" distributes over "and". It can look a bit strange since addition does not distribute Over multiplication.
A	Complement, Identity.

Simplify: $(A + C)(AD + AD) + AC + C$:

<u>Expression</u>	<u>Rule(s) Used</u>
$(A + C)(AD + AD) + AC + C$	Original Expression
$(A + C)A(D + D) + AC + C$	Distributive.
$(A + C)A + AC + C$	Complement, Identity.
$A((A + C) + C) + C$	Commutative, Distributive.
$A(A + C) + C$	Associative, Idempotent.
$AA + AC + C$	Distributive.
$A + (A + T)C$	Idempotent, Identity, Distributive.
$A + C$	Identity, twice.

UNIVERSAL GATES: NAND, NOR

Every other gate can be expressed or Symbolized as a combination of nand gates or nor gates.

NOR as a universal gate:-

$$\text{NOR: } Y = a' + b' \quad \text{OR} = \sim \text{NOR} = (a' + b')'$$

$$\text{NOT: } (a + a)'$$

$$\begin{aligned} \text{AND: } Y &= a.b \\ &= ((a.b))' \\ &= (a' + b')' \\ &= ((a+a)' + (b+b'))' \\ \text{NAND: } &= (((a+a)' + (b+b'))')' \end{aligned}$$


$$\begin{aligned} \text{EXOR: } Y &= a \text{ xor } b \\ &= ab' + a'b \\ &= ((ab' + a'b))' \\ &= ((ab')' . (a'b'))' \quad \because (x' + y') = x'.y' \\ &= ((a' + b) . (a + b'))' \quad \because (xy)' = x' + y' \\ &= \text{let } m = (a' + b) \quad n = (a + b') \\ &\quad (m.n)' = m' + n' \\ &= ((a' + b)' + (a + b'))' \quad \leftarrow \text{all NOR gates?} \\ &= (((a+a)' + b)' + (a + (b+b'))')' \end{aligned}$$









$$\text{EX-NOR: } (ab' + a'b)' = ab + a'b'$$

NAND as a universal gate:-

$$\begin{aligned} \text{NAND: } Y &= (a.b)' \\ \text{AND: } ((ab))' &= ((ab)' . (ab))' \\ \text{NOT: } (a.a)' & \\ \text{OR: } a+b &= ((a+b))' = (a'.b')' = ((a'b') . (a'b'))' \\ \text{NOR: } ((ab)' . (ab))' & \\ \text{EXOR: } (((a'b')' (ab'))')' & \\ \text{EX_NOR: } &\text{do it yourself} \end{aligned}$$

Logic Gates using only NAND Gates

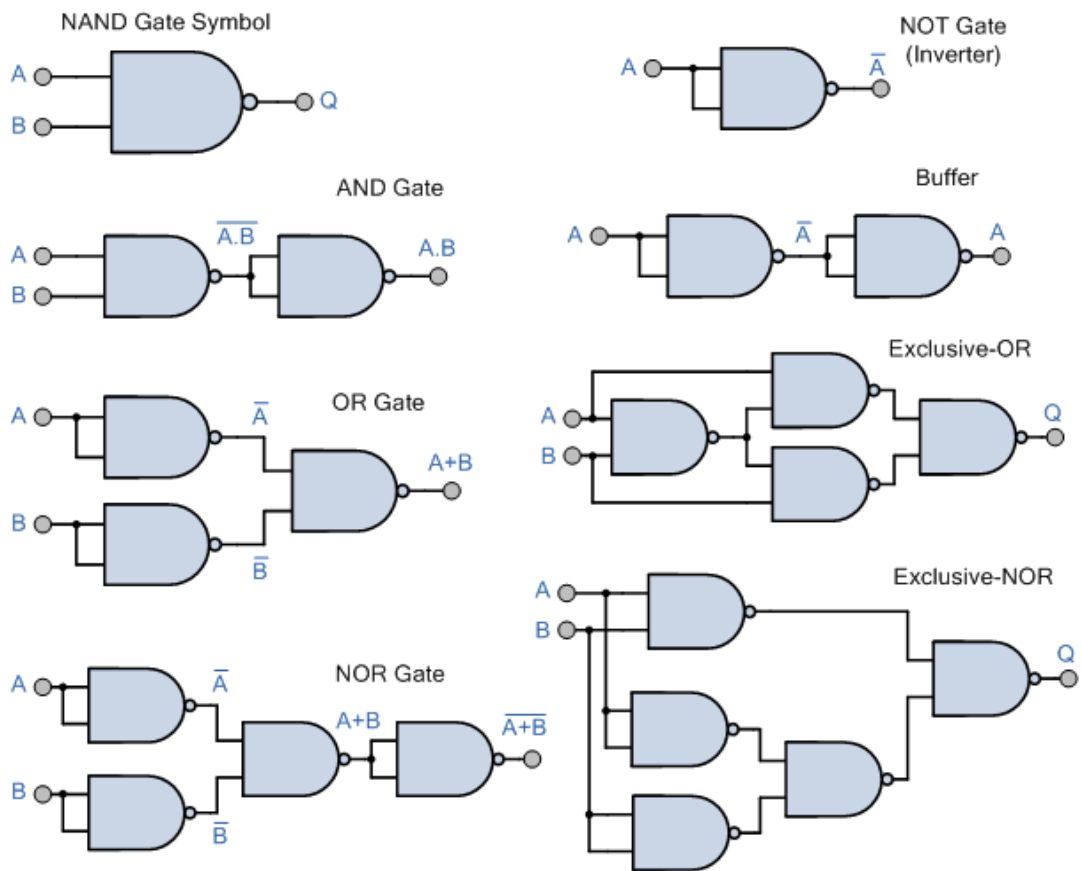

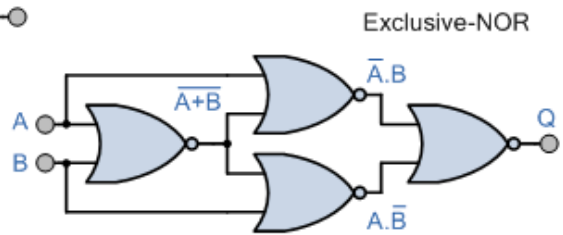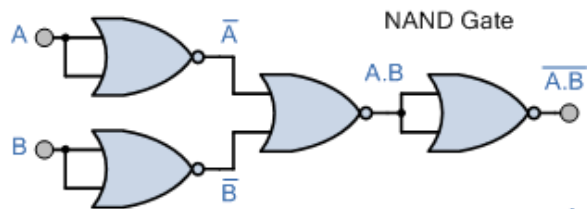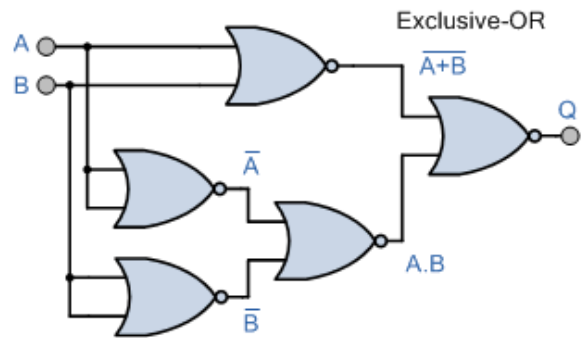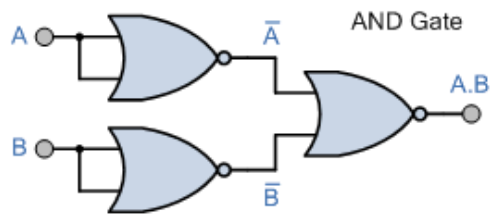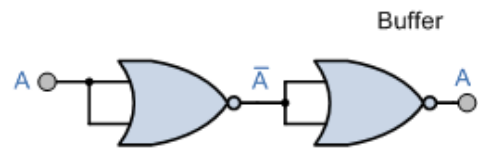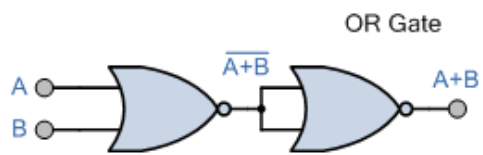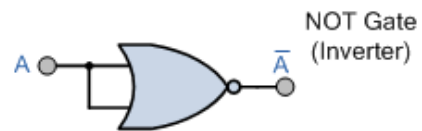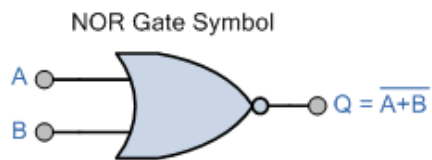

SOP = sum of products

$Y = a'b + bc$ each term ($a'b$, bc) is called a **Minterm**

POS = product of sums

$Y = (x'+z) \cdot (y+z')$ each term ($x'+z$) and ($y+z'$) is a **Maxterm**

Canonical or Standard Form

$Y(a,b,c) = ab + a'bc$ **not in** canonical form

$$ab(c+c') + a'bc$$

$abc + abc' + a'bc \leftarrow$ **is** a canonical SOP form

ex2: $Y(a,b,c,d) = ab + c'd'$

$$= ab + cd'$$

$$= ab(c+c')(d+d') + cd'(a+a')(b+b')$$

$$= ab(cd+cd'+cd'+c'd') + cd'(ab+a'b+ab'+a'b')$$

$$= abcd + abc'd + \underline{abcd'} + abc'd' + \textcolor{red}{abcd'} + a'bcd' + ab'cd' + a'b'cd' \text{ (term in red occurs more than once so only one copy is kept).}$$

$$= [abcd + abc'd + \underline{abcd'} + abc'd' + a'bcd' + ab'cd' + a'b'cd']$$

(is canonical SOP or standard SOP form of the given expression: $ab + cd'$)

$$Y(p,q,r) = (p+r') \cdot (p+q+r)$$

$$= (p + qq' + r') \cdot (p+q+r)$$

$$= (p+q+r') \cdot (p+q'+r') \cdot (p+q+r)$$

Is canonical **POS** form of the given expression.

$$P1) \quad X(a,b,c) = a'+b'$$

$$= a'(b+b')(c+c') + b'(a+a')(c+c')$$

$$= a'bc + a'b'c + a'bc' + a'b'c' +$$

$$ab'c + \textcolor{red}{a'b'c} + ab'c' + \textcolor{red}{a'b'c'}$$

$$P2) \quad Y(a,b,c)$$

$$= (a'+b')c$$

$$= (a'+b' + cc')(c + aa' + bb')$$

$$= (a'+b'+c)(a'+b'+c')(a+b+c)(a'+b+c)(a+b'+c)(\textcolor{red}{a'+b'+c'})$$

$$= (a'+b'+c)(a'+b'+c')(a+b+c)(a'+b+c)(a+b'+c)$$

Relation of Canonical Form or Standard form to Minterms or Maxterms:

EX1:

$$\begin{aligned}
 Y(a,b,c) &= ab + a'bc && \text{;not canonical form} \\
 &= ab(c+c') + a'bc \\
 &= abc + abc' + a'bc \leftarrow \text{is a canonical SOP form} \\
 &= m_7 + m_6 + m_3 \\
 &= \sum m(3,6,7)
 \end{aligned}$$

Here $Y(a,b,c)$ = Sum of products
 = contains minterms
 = each product is a minterm

a	b	c	
0	0	0	
0	0	1	
0	1	0	
0	1	1	$= a'bc = m_3$
1	0	0	
1	0	1	
1	1	0	$abc' = m_6$
1	1	1	$abc = m_7$

$$P = (a'+b'+c).(a'+b'+c').(a+b+c).(a'+b+c).(a+b'+c) = \text{Product of Sums}$$

a	b	c	
0	0	0	$= (a+b+c) = M_0$
0	0	1	
0	1	0	$= (a+b'+c) = M_2$
0	1	1	
1	0	0	$= (a'+b+c) = M_4$
1	0	1	
1	1	0	$= (a'+b'+c) = M_6$
1	1	1	$= (a'+b'+c') = M_7$

$$P = M_0 \cdot M_2 \cdot M_4 \cdot M_6 \cdot M_7 = \prod M(0,2,4,6,7)$$