

 


Sequential Circuits

Basics

 


Sequential Logic Circuits Tutorial

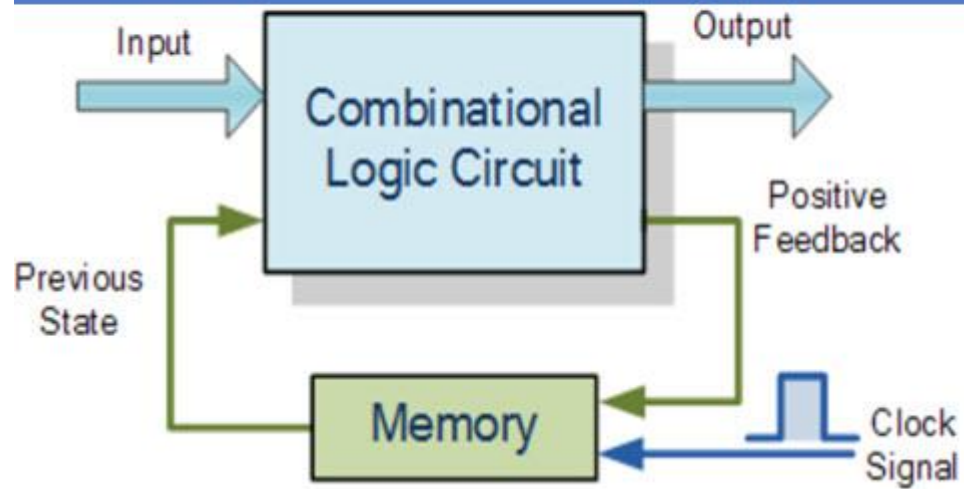

LATCHES and FLIP-FLOPS


Basic RS Latch using NOR gates:

 

S	R	Q	\overline{Q}
0	0	latch	latch
0	1	0	1
1	0	1	0
1	1	0	0

Basic RS Latch using NAND gates:

- Here the inputs R and S are active low

 


(a) Logic diagram

S	R	Q	Q'
1	0	0	1
1	1	0	1
0	1	1	0
1	1	1	0
0	0	1	1

 (b) Truth table

Gated RS latch

Only when the E (enable signal) is 1 the changes in the inputs are transferred to the output.




E	S	R	Q	\bar{Q}
0	0	0	latch	latch
0	0	1	latch	latch
0	1	0	latch	latch
0	1	1	latch	latch
1	0	0	latch	latch
1	0	1	0	1
1	1	0	1	0
1	1	1	0	0

SR Latch vs SR Flip-flop:

Usually a latch does not involve a clock; so the gated RS latch above is actually a SR flip-flop.

Timing diagram for a SR flip-flop:

 


D FLIP-FLOP



To avoid the illegal state in RS flip flop, we connect a NOT gate between

R and S inputs. That becomes a D flip flop.


Truth table D flip flop

 


D	CLK	Q(t+1)	Comments
1	↑	1	Set
0	↑	0	Reset

  

Circuit diagram of D flip flop:

 

(a) Logic diagram with NAND gates

 

(b) Graphical symbol


Q	D	Q(t+1)
0	0	0
0	1	1
1	0	0
1	1	1

(c) Transition table

Clocked D flip-flop

JK Flip-Flop:

 - The JK flip-flop does not have any illegal state like SR FF.
- The JK flip-flop has two inputs J and K which make it more useful than a D FF.
- The JK flip-flop has a toggle mode similar to the T FF which is very useful to design counters and state machines.



Truth Table

J	K	CLK	Q
0	0	↑	Q_0 (no change)
1	0	↑	1
0	1	↑	0
1	1	↑	\bar{Q}_0 (toggles)


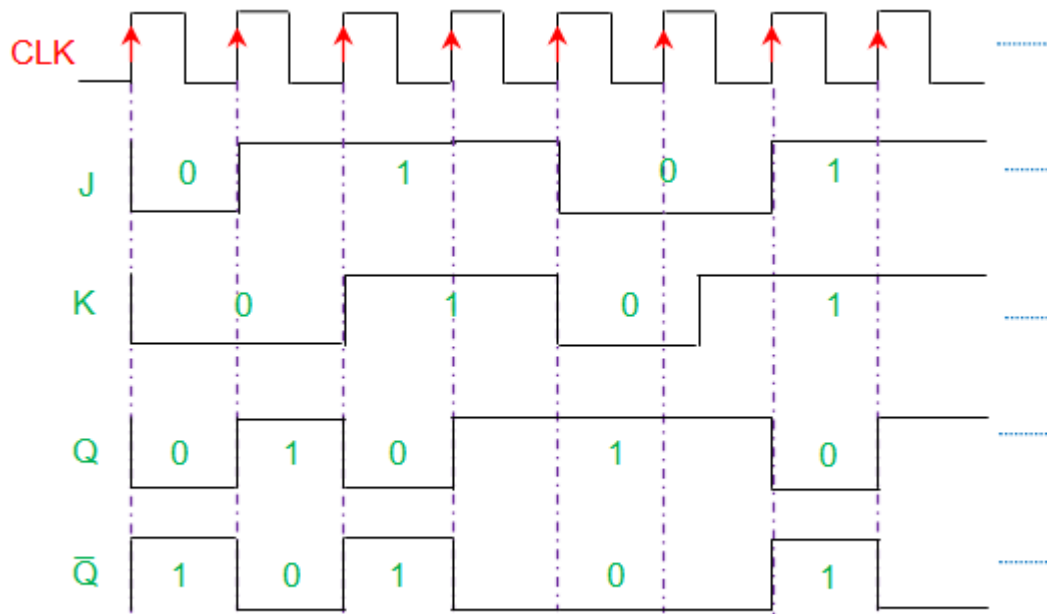
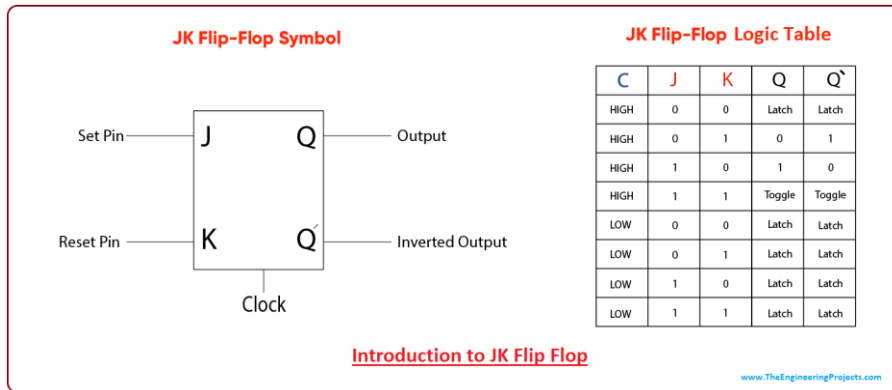


Figure 3 Timing diagram for positive edge-triggered JK flip-flop

 

Symbol: T Flip-flop


T Flip-Flop:

It has only one input T.

When $T=0$, no change in output.

When $T=1$, output reverses ($Q_{t+1} = \sim Q_t$)

T	Q	Q'
0	0	0
1	0	1
0	1	0
1	1	0

 

JK FF with Preset and Clear:


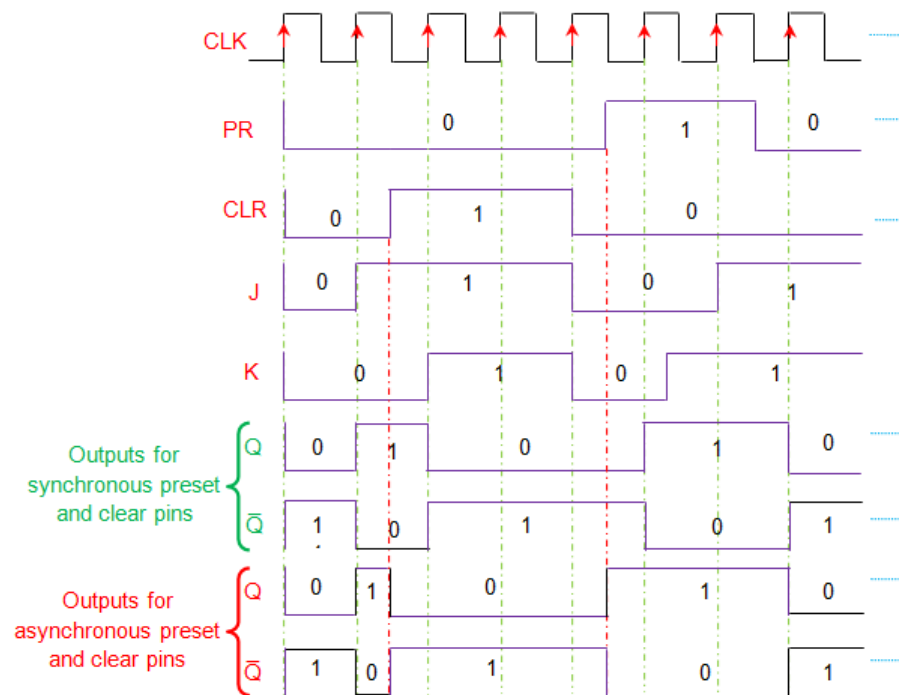
 


Figure 5 Waveforms for JK flip-flop with active high preset and clear inputs

JK Master-Slave FF:

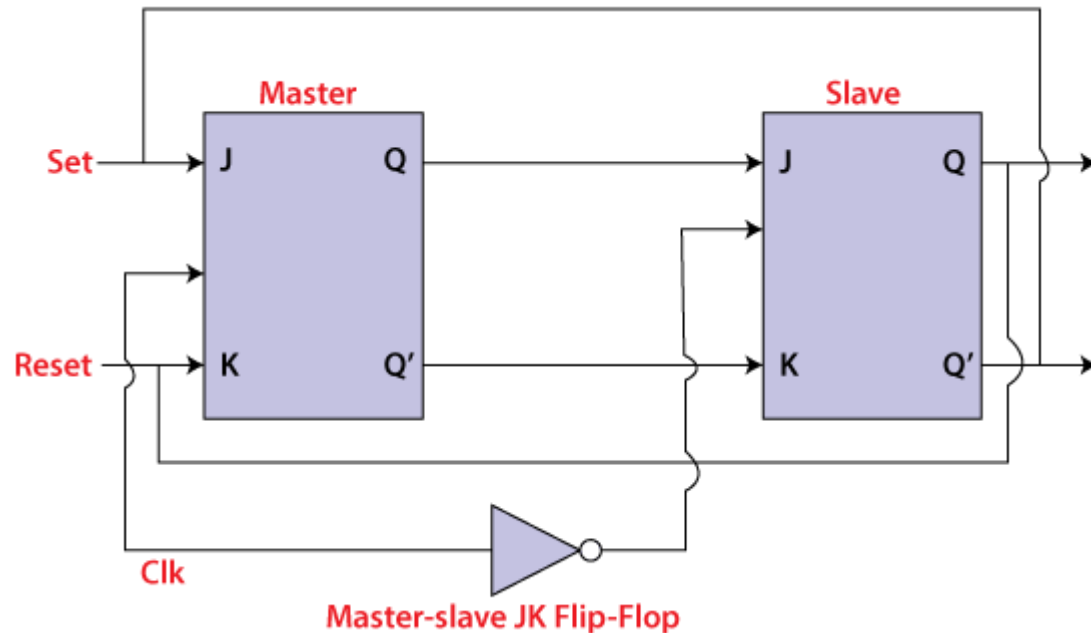


Working:

- When the clock pulse is true, the slave flip flop will be in the isolated state, and the system's state may be affected by the J and K inputs. The "slave" remains isolated until the CP is 1. When the CP set to 0, the master flip-flop passes the information to the slave flip flop to obtain the output.
- The master flip flop responds first from the slave because the master flip flop is the positive level trigger, and the slave flip flop is the negative level trigger.
- The output $Q'=1$ of the master flip flop is passed to the slave flip flop as an input K when the input J set to 0 and K set to 1. The clock forces the slave flip flop to work as reset, and then the slave copies the master flip flop.
- When $J=1$, and $K=0$, the output $Q=1$ is passed to the J input of the slave. The clock's negative transition sets the slave and copies the master.

- The master flip flop toggles on the clock's positive transition when the inputs J and K set to 1. At that time, the slave flip flop toggles on the clock's negative transition.
- The flip flop will be disabled, and Q remains unchanged when both the inputs of the JK flip flop set to 0.

Timing Diagram of a Master Flip Flop:

 

- When the clock pulse set to 1, the output of the master flip flop will be one until the clock input remains 0.
- When the clock pulse becomes high again, then the master's output is 0, which will be set to 1 when the clock becomes one again.
- The master flip flop is operational when the clock pulse is 1. The slave's output remains 0 until the clock is not set to 0 because the slave flip flop is not operational.
- The slave flip flop is operational when the clock pulse is 0. The output of the master remains one until the clock is not set to 0 again.
- Toggling occurs during the entire process because the output changes once in the cycle.

Truth Table: A Truth table shows how a logic circuits output responds to various combination of inputs.

Characteristics Table: it defines the next state of flip-flop in terms of flip-flop input and current state.

Excitation Table:it defines the flip-flop input variable as function of the current state and next state.

Somaiya Vidyavihar - Somaiya V...Inbox (7,625) - ravindraivekar...Summary of Types of Flip +

← → ↺ ⚡ Not secure | osp.mans.edu.eg/cs212/Seq_circuits_Summary_FF-types.htm#:~:text=The%20characteristic%20table%20for%20the,Q%20is%20set%20to%201.🔍 ⚙️ 🌐 📄

Apps 📱 37 Great Games For... 🎮 42 sr flip flop anima... 🎮 Double-Bottom Sto... 📊 The ultimate guide... 📖 A Comparison of A... 📅 5 steps for masterin... 🏥 Medical expenses o... 📈 Tax saving investm...

Table 1. Flip-flop types

FLIP-FLOP NAME	FLIP-FLOP SYMBOL	CHARACTERISTIC TABLE			CHARACTERISTIC EQUATION	EXCITATION TABLE			
SR		S	R	Q(next)	$Q_{(next)} = S + R'Q$ $SR = 0$	Q	Q(next)	S	R
		0	0	Q		0	0	0	X
		0	1	0		0	1	1	0
		1	0	1		1	0	0	1
		1	1	?		1	1	X	0
JK		J	K	Q(next)	$Q_{(next)} = JQ' + K'Q$	Q	Q(next)	J	K
		0	0	Q		0	0	0	X
		0	1	0		0	1	1	X
		1	0	1		1	0	X	1
		1	1	Q'		1	1	X	0
D		D		Q(next)	$Q_{(next)} = D$	Q	Q(next)	D	
		0		0		0	0	0	
		1		1		0	1	1	
						1	0	0	
T		T		Q(next)	$Q_{(next)} = TQ' + T'Q$	Q	Q(next)	T	
		0		Q		0	0	0	
		1		Q'		0	1	1	
						1	0	1	
						1	1	0	

Each of these flip-flops can be uniquely described by its graphical symbol, its characteristic table, its characteristic equation or excitation table. All flip-flops have output signals Q and Q'.

Desktop 11:45 05-10-2024

(Bigger Image uploaded as a separate file).

Inputs		Outputs	
		Present State	Next State
S	R	Q_n	Q_{n+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	invalid	
1	1	invalid	

Truth Table of SR Flip-Flop

Outputs		Inputs	
Present State	Next State	S	R
Q_n	Q_{n+1}	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

Excitation Table of SR Flip-Flop

Inputs		Outputs	
		Present State	Next State
J	K	Q_n	Q_{n+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

Truth Table of JK Flip-Flop

Outputs		Inputs	
Present State	Next State	J	K
Q_n	Q_{n+1}	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

Excitation Table of JK Flip-Flop

Input	Outputs	
	Present State	Next State
D	Q_n	Q_{n+1}
0	0	0
0	1	0
1	0	1
1	1	1

Truth Table of D Flip-Flop

Outputs		Input
Present State	Next State	
Q_n	Q_{n+1}	D
0	0	0
0	1	1
1	0	0
1	1	1

Excitation Table of D Flip-Flop

Input	Outputs	
	Present State	Next State
T	Q_n	Q_{n+1}
0	0	0
0	1	1
1	0	1
1	1	0

Truth Table of T Flip-Flop

Outputs		Input
Present State	Next State	
Q_n	Q_{n+1}	T
0	0	0
0	1	1
1	0	1
1	1	0

Excitation Table of T Flip-Flop

Conversion Table

Truth Table of the
Desired Flip-Flop

Excitation Table of
the Given Flip-Flop

Truth Table of D Flip-flop

Input	Outputs	
	Present State	Next State
D	Q_n	Q_{n+1}
0	0	0
0	1	0
1	0	1
1	1	1

Excitation Table of SR Flip-flop

Outputs		Inputs	
Present State	Next State		
Q_n	Q_{n+1}	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

SR to D Conversion Table


D Input	Outputs		SR Inputs	
	Present State	Next State		
D	Q_n	Q_{n+1}	S	R
0	0	0	0	X
0	1	0	0	1
1	0	1	1	0
1	1	1	X	0

D \ Q _n	0	1
0	0 ⁰	0 ¹
1	1 ²	X ³

$S = D$

D \ Q _n	0	1
0	X ⁰	1 ¹
1	0 ²	0 ³

$R = \bar{D}$

 

Conversion of D flip-flop to JK Flip flop

Step1: Write the characteristic table of the desired FF (JK)

Step2: Excitation table for given flip flop (D)

Step3: Combine the two and draw K map

J	K	Q	Q+1	D
0	0	0	0	0
0	0	0	0	0
0	1	0	0	0
0	1	0	0	0
1	0	0	1	1
1	0	1	1	1
1	1	1	0	0
1	1	0	1	0

$$D = K'Q + JQ'$$

0	1	0	0
1	1	0	1

$$D = K'Q + JQ'$$